

A Simple Implementation

EE380, Spring 2018

Hank Dietz

<http://aggregate.org/hankd/>

Where Is This Stuff?

- Not in the text per se...
- Primary reference is:

<http://aggregate.org/EE380/refss.html>

- Textbook appendix B has EE280 review stuff...

A Dumb Implementation

- A design like I learned as an undergrad...
 - Can be built with a pile of TTL parts
 - Can execute MIPS instructions
 - Slow; many clock cycles per instruction
- The key parts:
 - Memory
 - Processor
 - I/O – which we'll ignore for now...


Our Favorite Gates

- In EE280, you never used one of these:




but they help keep signals digital...

- In EE380, we use lots of these:

 


to make **bus** and **mux** structures...


Tri-State (& Open Collector)

 

Driver

 

Tri-State Driver

 


| In | enable | A | B | out |
|----|--------|-----|-----|--------|
| X | 0 | off | off | Z |
| 0 | 1 | off | on | 0 |
| 1 | 1 | on | off | 1 |
| | | on | on | short! |


Open Collector replaces A with a resistor

TTL Input floats high; CMOS doesn't


Processor/Memory Interface

 


A bit Of SRAM (D Flip Flop)

 

A Simple Memory

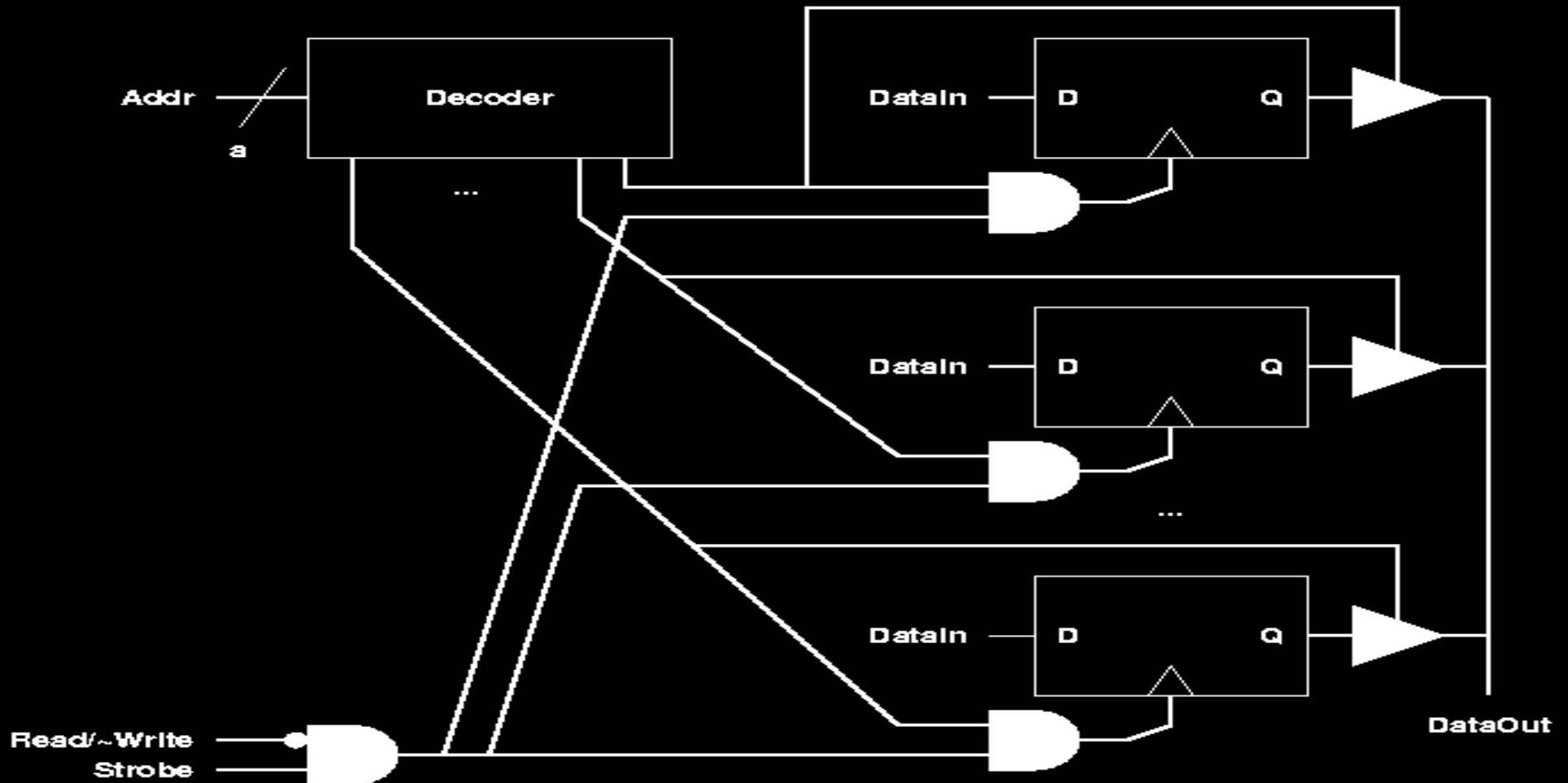


A bit Of DRAM

 

- Data to V_{cc} to store 1
- Data to Gnd to store 0
- Dump charge, amplify, & threshold to read...
 - Analog – slow & noise sensitive
 - Destructive (need to refresh value)
- Charge slowly leaks (need to refresh value)

Inside The Processor

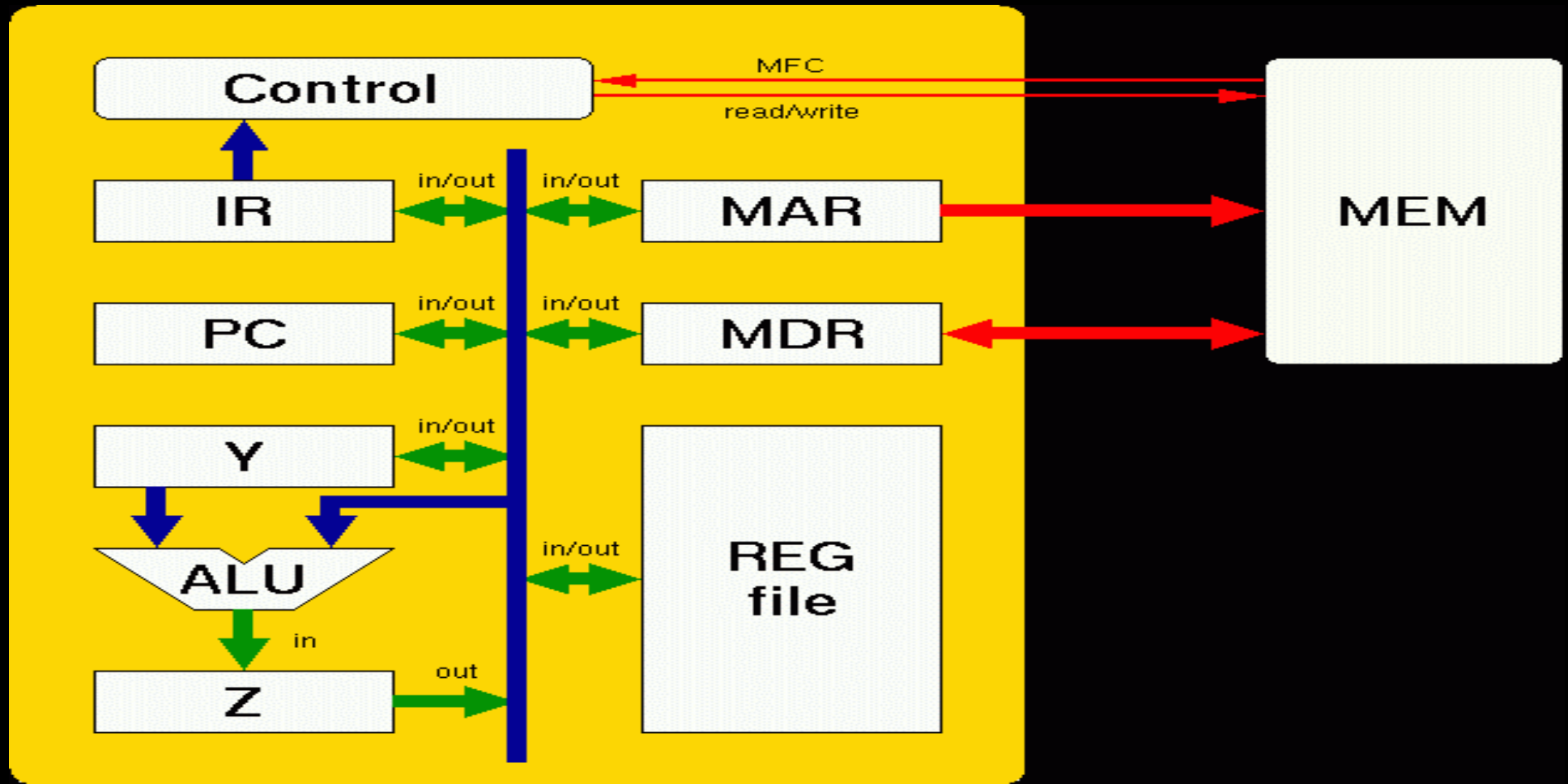

| REGISTER control signal | Effect |
|-------------------------|--|
| ALUadd | Configures the ALU to add its inputs |
| ALUand | Configures the ALU to bitwise AND its inputs |
| ALUxor | Configures the ALU to bitwise eXclusive OR its inputs |
| ALUor | Configures the ALU to bitwise OR its inputs |
| ALUsl | Configures the ALU to shift left logical; the result is (bus << Y) |
| ALUslt | Configures the ALU to compare its inputs; the result is (Y < bus) |
| ALU srl | Configures the ALU to shift right logical; the result is (bus >> Y) |
| ALUsub | Configures the ALU to subtract the bus input from Y |
| CONST(<i>value</i>) | Places the constant <i>value</i> onto the bus |
| HALT | Halt the machine (stop the simulator without error) at the end of the current state |
| IRaddout | Tri-state enables the portion of the Instruction Register that contains the (26 bit, MIPS "J" format) address, along with the top 6 bits of the Program Counter, to be driven onto the bus |
| IRimmedout | Tri-state enables the portion of the Instruction Register that contains the (16 bit, MIPS "I" format) 2's complement immediate value to be sign-extended to 32 bits and driven onto the bus |
| IRin | Latches the bus data into the Instruction Register at the trailing edge of the clock cycle |
| IRoffsetout | Tri-state enables the Instruction Register's shifted and sign extended value from the offset field to be driven onto the bus (used for branches) |
| JUMP(<i>label</i>) | Microcode jump to <i>label</i> |
| JUMPonop | Microcode jump to label named like the opcode; e.g., if an "Addi" is in the IR, jumps to the microcode label Addi |
| MARin | Latches the bus data into the Memory Address Register at the trailing edge of the clock cycle |
| MARout | Tri-state enables the Memory Address Register's output to be driven onto the bus |
| MDRin | Latches the bus data into the Memory Data Register at the trailing edge of the clock cycle |
| MDRout | Tri-state enables the Memory Data Register's output to be driven onto the bus |
| MEMread | Initiate a memory read from the address in the MAR; here, you may assume that the memory will take 2 clock cycles to respond |
| MEMwrite | Initiate a memory write using the data in the MDR and the address in the MAR; in this simple design, you may assume that a memory write takes precisely 1 clock cycle |
| PCin | Latches the bus data into the Program Counter at the trailing edge of the clock cycle |
| PCinif0 | Only if the value in Z is zero, latch the bus data into the Program Counter at the trailing edge of the clock cycle |
| PCout | Tri-state enables the Program Counter's output to be driven onto the bus |
| REGin | Latches the bus data into whichever register is selected by SELrs, SELrt, or SELrd; the value is latched at the trailing edge of the clock cycle |
| REGout | Tri-state enables the output of whichever register is selected by SELrs, SELrt, or SELrd; the selected value is driven onto the bus |
| SELrs | Selects the rs field of the IR to be used to control the register file's decoder |
| SELrt | Selects the rt field of the IR to be used to control the register file's decoder |
| SELrd | Selects the rd field of the IR to be used to control the register file's decoder |
| UNTILmfc | Repeat this state until the memory has issued a memory fetch complete signal, indicating that the fetched value will be valid to read from the MDR in the next clock cycle |
| Yin | Latches the bus data into the Y register at the trailing edge of the clock cycle; this register is needed because, with only one bus, one of the two operands for a binary operation (e.g., Add) must come from somewhere other than the bus |
| Yout | Tri-state enables the Y register's output to be driven onto the bus |
| Zin | The ALU is always producing a result, but we only make note of that result if we latch the ALU's output into the Z register at the trailing edge of the clock cycle |
| Zout | Tri-state enables the Z Register's output to be driven onto the bus |

Control Logic

- A big state machine (spec. by names)
 - Begins by fetching instruction
 - Decoding instruction sends us to particular instruction's state sequence
 - Ends by going to fetch next instruction
- Instruction decode logic
 - when mask match statename*
 - Applied in state with **JUMPONOP**
 - *if ((IR & mask) == match) goto statename;*

Instruction Fetch Sequence

- Not dependent on instruction type – can't be
- Also does $PC += 4$

```
Start: PCout, MARin, MEMread, Yin  
      CONST(4), ALUadd, Zin, UNTILmfc  
      MDROUT, Irin  
      JUMPONOP, Zout, Pcin  
      HALT /* illegal inst. */
```

MIPS Register Add

- `add $rd,$rs,$rt`
- Means $rd = rs + rt$

Add: SELrs,REGout,Yin
SELrt,REGout,ALUadd,Zin
Zout,SELrd,REGin,JUMP(Start)

MIPS Register And

- `and $rd,$rs,$rt`
- Means $rd = rs \& rt$

`And: SELrs,REGout,Yin
SELrt,REGout,ALUand,Zin
Zout,SELrd,REGin,JUMP(Start)`

MIPS Load Word

- `lw $rt,immed($rs)`
- Means $rt = \text{mem}[immed + rs]$

Lw: SELrs,REGout,Yin
IRIMMEDout,ALUadd,Zin
Zout,MARin,MEMread
UNTILmfc
MDRout,SELrt,REGin,JUMP(Start)

MIPS Store Word

- `sw $rt,immed($rs)`
- Means $\text{mem}[\text{immed} + \text{rs}] = \text{rt}$
- Don't have to wait for write to complete

Sw: SELrt,REGout,MDRin
SELrs,REGout,Yin
IRIMMEDout,ALUadd,Zin
Zout,MARin,MEMwrite,JUMP(Start)

Timing

- Clock period determined by slowest path in any state – try to minimize variation
- Number of clock cycles/instruction (CPI) is determined by counting
 - Not just count of states passed through
 - Time passed waiting counts (UNTILmfc)
- Clock period and CPI usually trade off; higher Hz often achieved by higher CPI

Clock Period

- Assume the critical state is:

$SEL_{rt}, REG_{out}, MDR_{in}, ALU_{add}, Z_{in}$

- The paths are:

$SEL_{rt} > REG_{out} > MDR_{in}$

$SEL_{rt} > REG_{out} > ALU_{add} > Z_{in}$

Reducing Clock Period

- Clock speed can be increased by replacing:

`SELrt, REGout, MDRin, ALUadd, Zin`

- With:

`SELrt, REGout, MDRin`

`MDRout, ALUadd, Zin`

Counting CPI

- Instruction fetch time counts
- Time between MEMread and UNTILmfc

```
Lw: SELrs,REGout,Yin +1
    IRIMMEDout,ALUadd,Zin +1
    Zout,MARin,MEMread +1
    UNTILmfc +?
    MDRout,SELrt,REGin,JUMP(Start) +1
```

A Verilog Implementation

- Design for simulation, not rendering HW
- Key ideas:
 - ``define` control signals & constants
 - `module memory(...);`
Models main memory
 - `module simple(halt, reset, clk);`
Models the complete processor
 - `module bench;`
Drives the simulation

Verilog Simulation

- ``define` control signals & constants
- `module memory(...);`
Models main memory
- `module simple(halt, reset, clk);`
Models the complete processor
- `module bench;`
Drives the simulation

Verilog Simulation

- Could go very low level, e.g.:

```
module DFF(q, d, clk, reset);  
input d, clk, reset;  
output reg q;  
always @(posedge reset or  
        negedge clk)  
    if (reset) q = 1'b0; else q = d;  
Endmodule
```


Verilog Simulation

- Don't have to go low level:

<http://aggregate.org/EE380/simplev.html>

- Don't have to feed it raw bits either;
here's a (slightly mutant) MIPS assembler:

<http://aggregate.org/EE380/simplev.html>